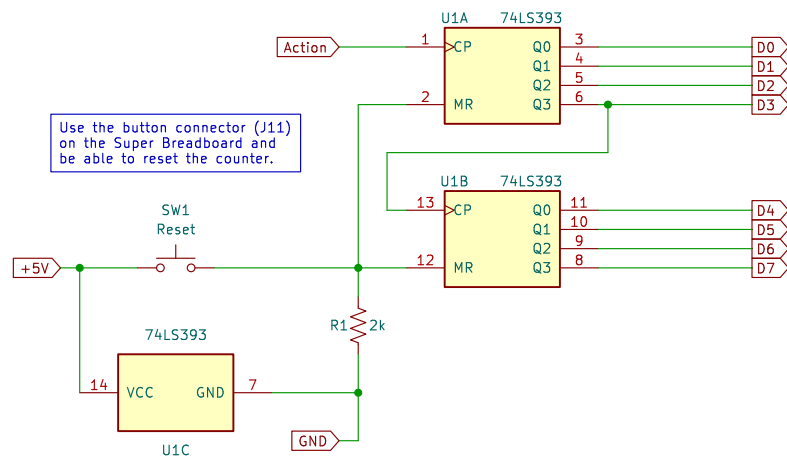


Wire the output of the Action-button of the 8-bit Workbench to the clock input of the IC (use connector J7 on the Super Breadboard). Make sure the Action -> Clock jumper (JP10 on the Workbench) is NOT set. Then this button can be used to increment the counter.

Option: add a LED to this Action by wiring its signal to the + of the LED on the Super Breadboard, make sure the - is attached to ground.

Attach the Super Breadboard to the 8-bit Workbench and wire the IC output to the output connector (J7) on the Super Breadboard.



A simple example circuit that can be build on the Super Breadboard: an 8-bit counter with reset functionality. Only a 74LS393 chip and a 2k resistor is needed.

Switch between hexadecimal and octal counting on the 8-bit Workbench. See if you can extend this circuit with a 555 timer IC, so the counter counts automatically.

Sheet: /
File: PrototypeExample.kicad_sch

Title: Prototype example for the Super Breadboard

Size: A4 Date: 2025-08-27

KiCad E.D.A. eeschema 7.0.5-0

Rev: 1

Id: 1/1